
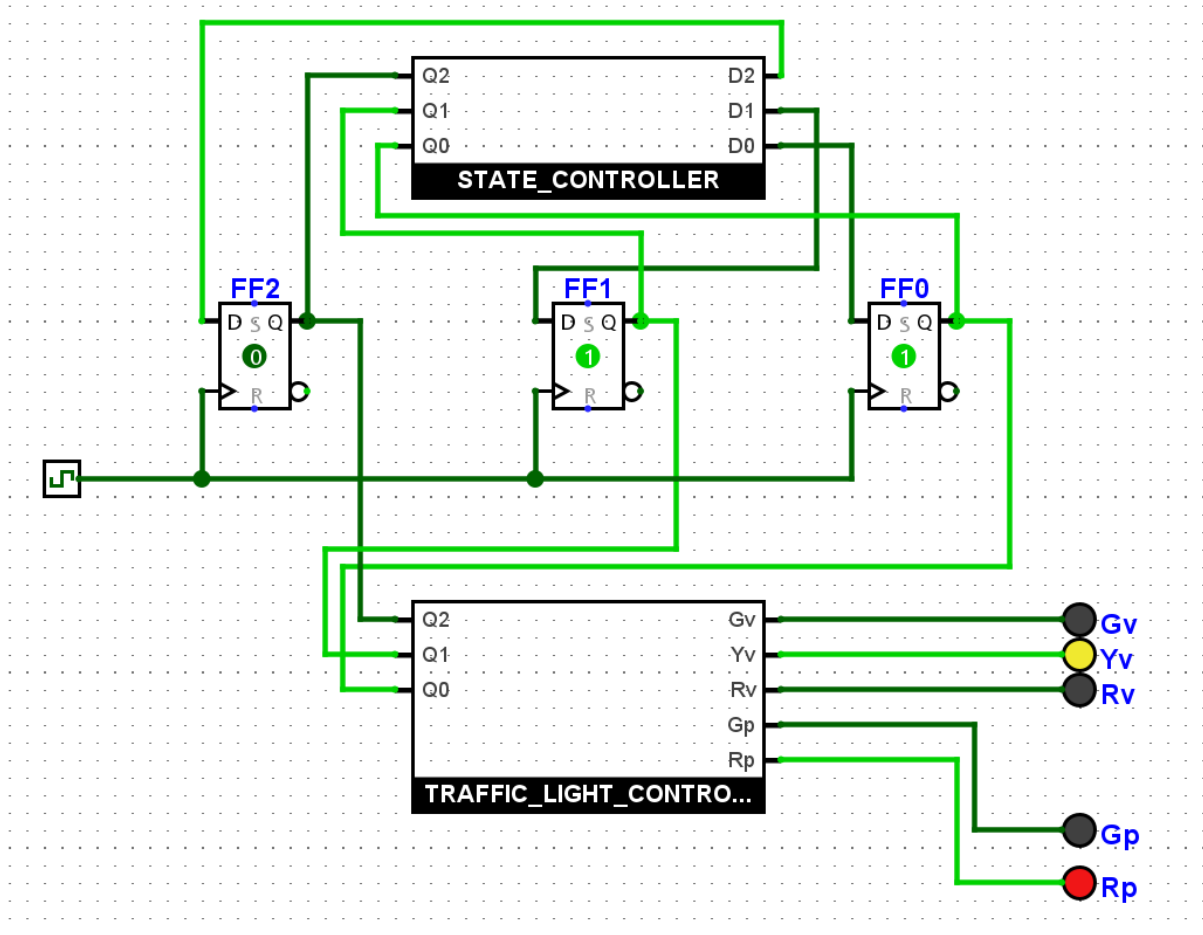


System Design / chronogram

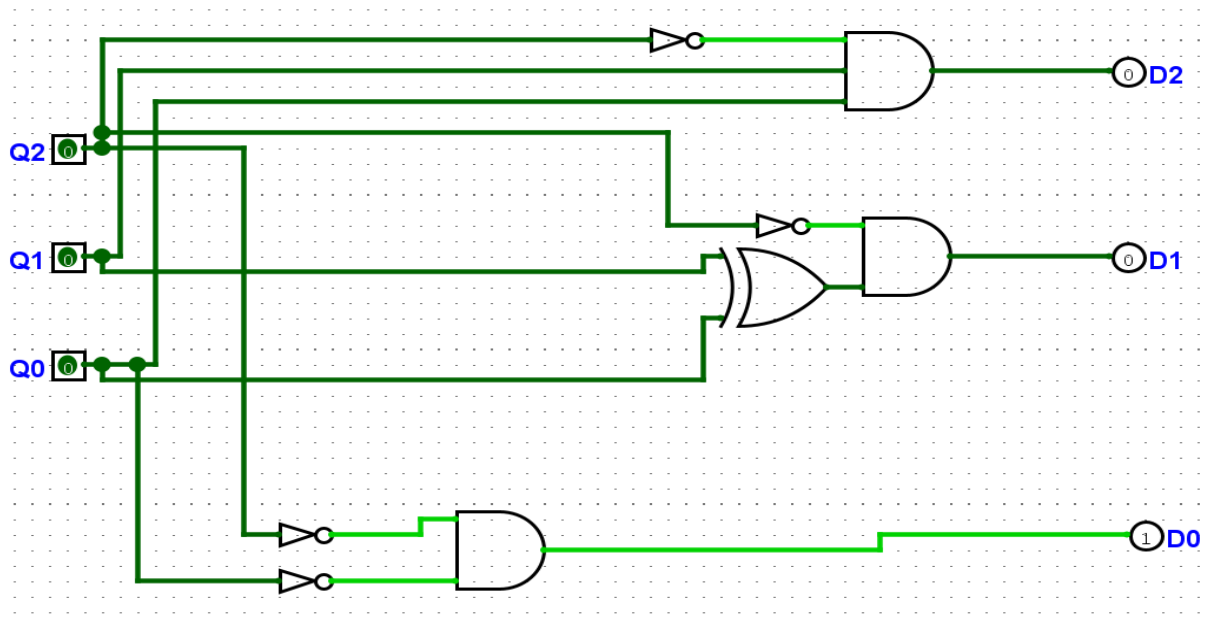
- The structure of our circuit is as follows:




- The State controller above is designed like this:



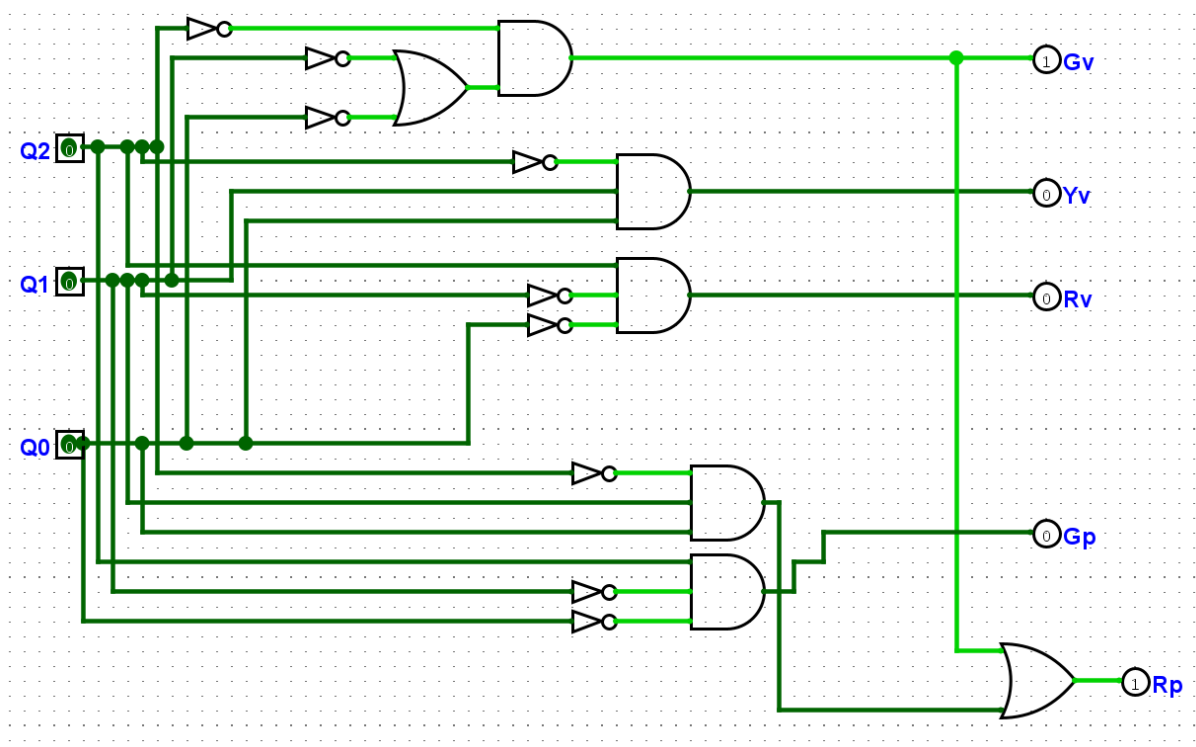- And the Traffic light controller is designed like this:




- Here are two phases of the Chronogram:

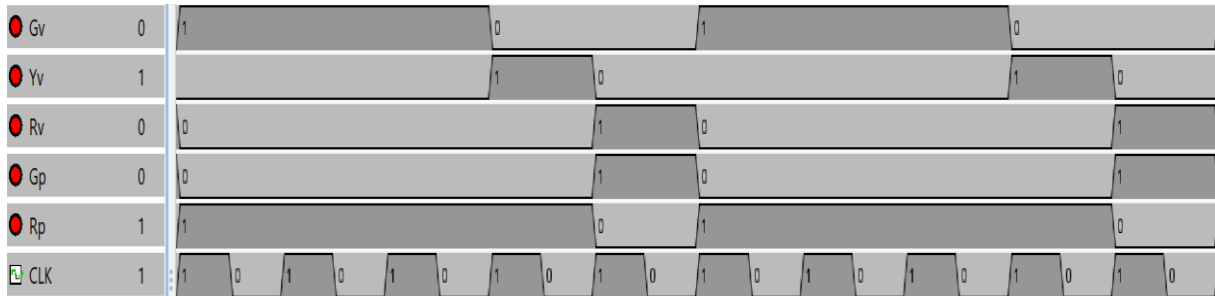


- The three states of the circuit :

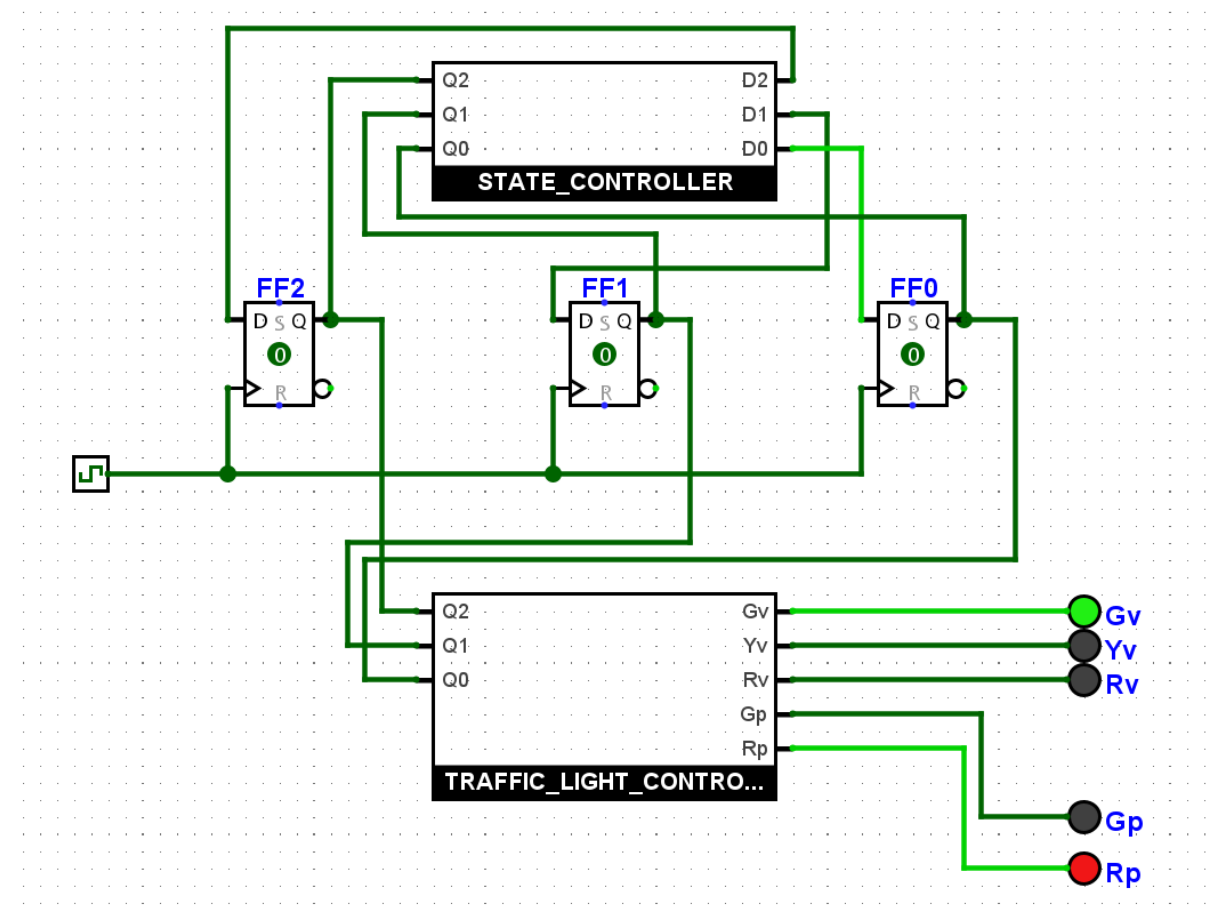Green light for vehicles, and red light for pedestrians:



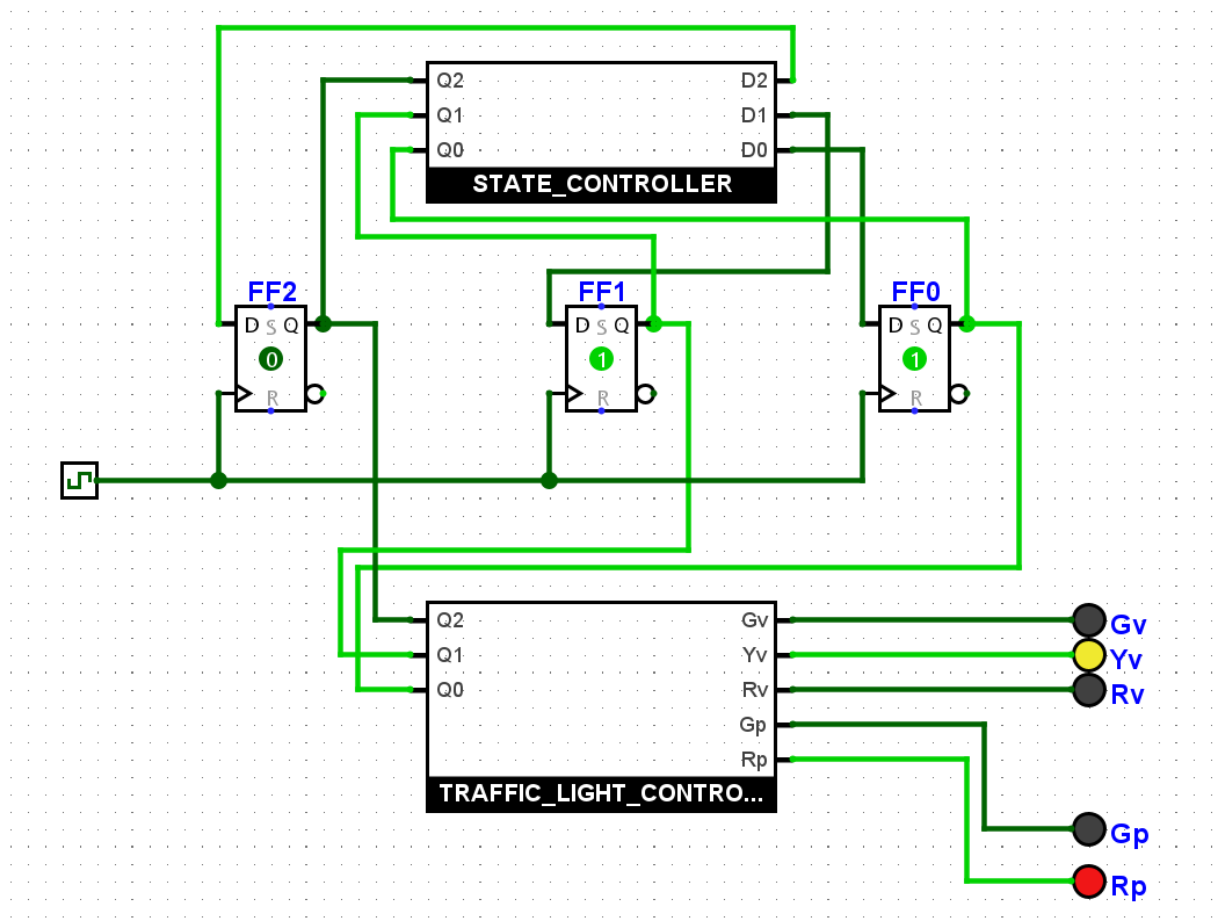Yellow light for vehicles, and red light for pedestrians:



And finally, Red light for vehicles, and green light for pedestrians:

