

# Traffic Light Control System Design

Digital Logic Design Project

September 2, 2025

## 1 Objective

The objective of this project is to design and simulate a traffic light control system. The system utilizes a clock, D Flip-Flops for sequential logic, and combinational logic for state transitions. The design specifications are as follows:

- Three states for vehicle lights: Red, Yellow, Green.
- Two states for pedestrian lights: Red, Green.

## 2 State Definitions and Timing

The system operates through three primary states with the following durations:

- **State A:** Vehicle light Green, Pedestrian light Red — 6 seconds.
- **State B:** Vehicle light Yellow, Pedestrian light Red — 2 seconds.
- **State C:** Vehicle light Red, Pedestrian light Green — 2 seconds.

To simplify the circuit design, a clock with a cycle duration of 2 seconds (frequency = 0.5 Hz) is used. The states are mapped to clock cycles as follows:

- S0: A (first 2 seconds)
- S1: A (second 2 seconds)
- S2: A (third 2 seconds)
- S3: B (2 seconds)
- S4: C (2 seconds)

Thus, State A remains active for 6 seconds (3 clock cycles), while States B and C are active for 2 seconds each.

**Note:** In the Logisim simulation file, the clock frequency must be set to 0.5 Hz before enabling the clock.


## 3 State Encoding and Diagram

The system requires 5 states, which are encoded using 3 bits ( $Q_2Q_1Q_0$ ). The state assignments are:

- S0: 000
- S1: 001
- S2: 010
- S3: 011
- S4: 100

Three D Flip-Flops are used to store the current state ( $Q_2Q_1Q_0$ ) and compute the next state ( $D_2D_1D_0$ ).

### 3.1 State Diagram

 

### 4 Next State Table

The next state and output values are determined from the current state as shown in Table 1.

Table 1: Next State and Output Table

Current State			Next State			Outputs				
$Q_2$	$Q_1$	$Q_0$	$D_2$	$D_1$	$D_0$	$G_v$	$Y_v$	$R_v$	$G_p$	$R_p$
0	0	0	0	0	1	1	0	0	0	1
0	0	1	0	1	0	1	0	0	0	1
0	1	0	0	1	1	1	0	0	0	1
0	1	1	1	0	0	0	1	0	0	1
1	0	0	0	0	0	0	0	1	1	0

Subscripts:  $v$  for vehicle,  $p$  for pedestrian.

### 5 Flip-Flop Equations

Using the Sum of Products method on the next state table, the following equations for the D Flip-Flop inputs are derived:

$$\begin{aligned}
 D_2 &= Q'_2 \cdot Q_1 \cdot Q_0 \\
 D_1 &= Q'_2 \cdot Q'_1 \cdot Q_0 + Q'_2 \cdot Q_1 \cdot Q'_0 = Q'_2 \cdot (Q_1 \oplus Q_0) \\
 D_0 &= Q'_2 \cdot Q'_1 \cdot Q'_0 + Q'_2 \cdot Q_1 \cdot Q'_0 = Q'_2 \cdot Q'_0
 \end{aligned}$$

### 6 Output Equations

Similarly, the output equations are derived from the next state table:

$$\begin{aligned}
 G_v &= Q'_2 \cdot Q'_1 \cdot Q'_0 + Q'_2 \cdot Q'_1 \cdot Q_0 + Q'_2 \cdot Q_1 \cdot Q'_0 \\
 &= Q'_2 \cdot Q'_1 + Q'_2 \cdot Q_1 \cdot Q'_0 = Q'_2(Q'_1 + Q_1 \cdot Q_0) \\
 &= Q'_2(Q'_1 + Q'_0) \\
 Y_v &= Q'_2 \cdot Q_1 \cdot Q_0 \\
 R_v &= Q_2 \cdot Q'_1 \cdot Q'_0 \\
 G_p &= Q_2 \cdot Q'_1 \cdot Q'_0 \\
 R_p &= Q'_2 \cdot Q'_1 \cdot Q'_0 + Q'_2 \cdot Q_1 \cdot Q_0 = G_v + Q'_2 \cdot Q_1 \cdot Q_0
 \end{aligned}$$

## **7 System Design and Chronogram**

The complete system design, chronogram (timing diagram), simulation examples, and waveform output are detailed in the accompanying documentation.

## **8 Logical Analysis**

Flip-Flops are fundamental components in sequential logic circuits, providing state storage and management. They enable precise state transitions synchronized with clock pulses. The combination of sequential logic (Flip-Flops) and combinational logic (for next-state and output determination) is essential for achieving reliable and efficient circuit behavior in this traffic light control system.